

JADAVPUR UNIVERSITY

Faculty of Engineering & Technology

Electronics Engg. Laboratory

Name TATHAGATA SOR

Class CSE-VG1 Sec. A1 Roll No. 002310501030

Date of Experiment 15/01/24 Date of Submission 22/01/24

Marks Obtained _____ Signature of Examiner _____

NAME

CO-WORKER

ROLL

Shyam Sundar Karmakar

002310501025

Samim Sekh

002310501026

Pratyay Kar

002310501027

Joyesmit Pal

002310501028

Abir Chakraborty

002310501029

Anirudh Modi

002310501031

Experiment No. 03

Commence at 11:00 AM

Completed at 2:00 PM


Name of Teacher concerned _____

TITLE: Study of diode rectifier circuits with capacitor filter.

OBJECT: To study the ripple characteristics and to observe the output waveform of a full wave rectifier with capacitor filter against varying Load current.

Theory:- Full wave rectifier consists of two half wave rectifier circuits with common load. They are connected in such a way that conduction takes place through two diodes in alternate half cycles, and current through the load is sum of two currents. Filters are used to reduce the ripples.

Circuit Diagram:-

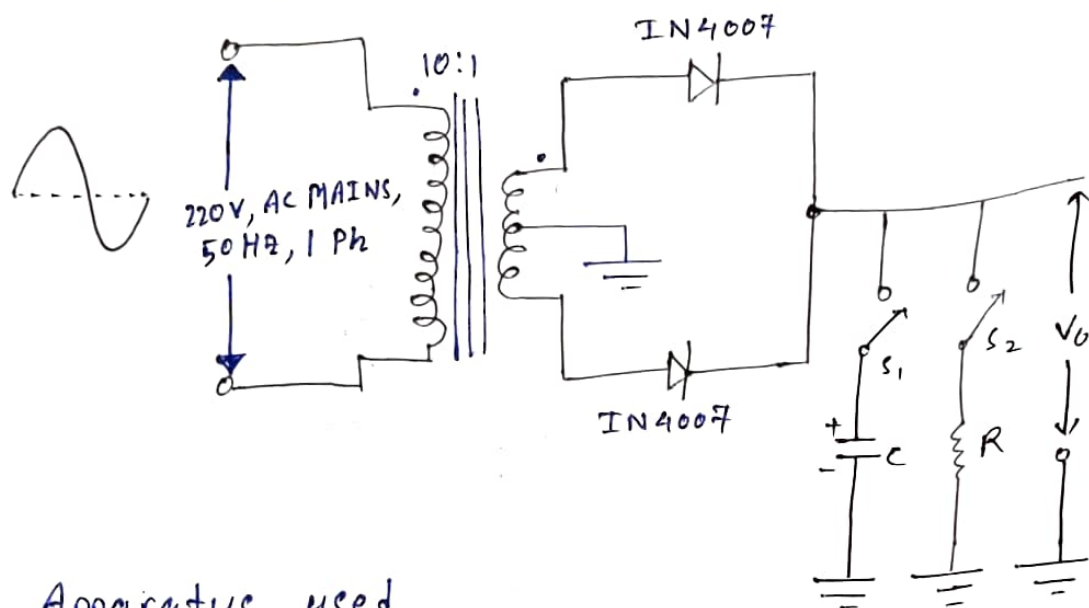

Apparatus used

- 1) Bread Board
- 2) Diodes (IN4007)
- 3) Resistors ($200\ \Omega$ each)
- 4) Capacitor ($1000\ \mu\text{F}$)
- 5) Multi-meter
- 6) Oscilloscope

OBSERVATION TABLE

$$C = 1000 \mu F, f = 50 \text{ Hz}$$

Sl. No.	R_L (in Ω)	V_{pp} (in V)	$V_{rms} = \frac{V_{pp}}{2.53}$	V_{dc} by voltmeter with capacitor	Ripple factor $= \frac{V_{rms}}{V_{dc}}$	Calculated Ripple factor $R = \frac{1}{4\sqrt{3}fCR_L}$
1)	200	0.64	0.1848	15.85	0.0116	0.0144
2)	400	0.32	0.0924	16.20	0.0057	0.0072
3)	600	0.22	0.0635	16.32	0.0039	0.0048
4)	800	0.17	0.0491	16.52	0.0029	0.0036

$$V_{ac} = 36 \text{ V}, V_{ac}(\text{rectified}) = 16 \text{ V}$$

Time periods

Non rectified sine wave: 20 ms

Rectified wave: 10 ms

Filtered wave: 10 ms

Graph of waveform

Fullwave Rectifier with Capacitor Filter

