

Laboratory Attendance Slip

Electrical Engineering Department
Jadavpur University

25, 33 Absent



Class CSE-I Sec A/A Experiment No. 04 Lab. M/R Date 30.10.2023

Name of the Experiment Power & Power factor characteristics of Fluorescent lamp.

Roll Nos. Assigned (25) 26, 27, 28, 29, 30, 31, 32, (33) 34, 35, 36,

Signature of Teacher.....

Date 30-10-23

JADAVPUR UNIVERSITY

Faculty of Engineering & Technology

....Electrical... Engg. Laboratory

Name.....TATHAGATA SVR.....

Class CSE-V Sec. A1 Roll No. 202310501030

Date of Experiment.....30/10/2023..... Date of Submission.....06/11/2023.....

Marks Obtained..... Signature of Examiner.....

NAME _____

CO-WORKER

ROLL

..... EKORSHI CHAUDHURI

002310501034...

ANIRVODH MODE

0023.10.50.1031.....

KUSHAL BERA

002210501035...

...M.D.V.R.Y.A.....S.A.H.A.

0.02310501036....

..P.R.A.T.Y.A.Y.....K.A.R.

0023 10501027...

Experiment No. 04

Commence at.....

Completed at.....

Name of Teacher concerned

TITLE: POWER & POWER FACTOR CHARACTERISTICS
OF FLUORESCENT LAMP


OBJECT: To obtain the power consumption and power factor of a fluorescent lamp when operated at different voltages.

EXPERIMENT NO: 04

TITLE:- POWER AND POWER FACTOR CHARACTERISTICS OF FLUORESCENT LAMP

OBJECTIVE:- To obtain the power consumption and power factor of a fluorescent lamp when operated at different voltages.

CIRCUIT DIAGRAM:-

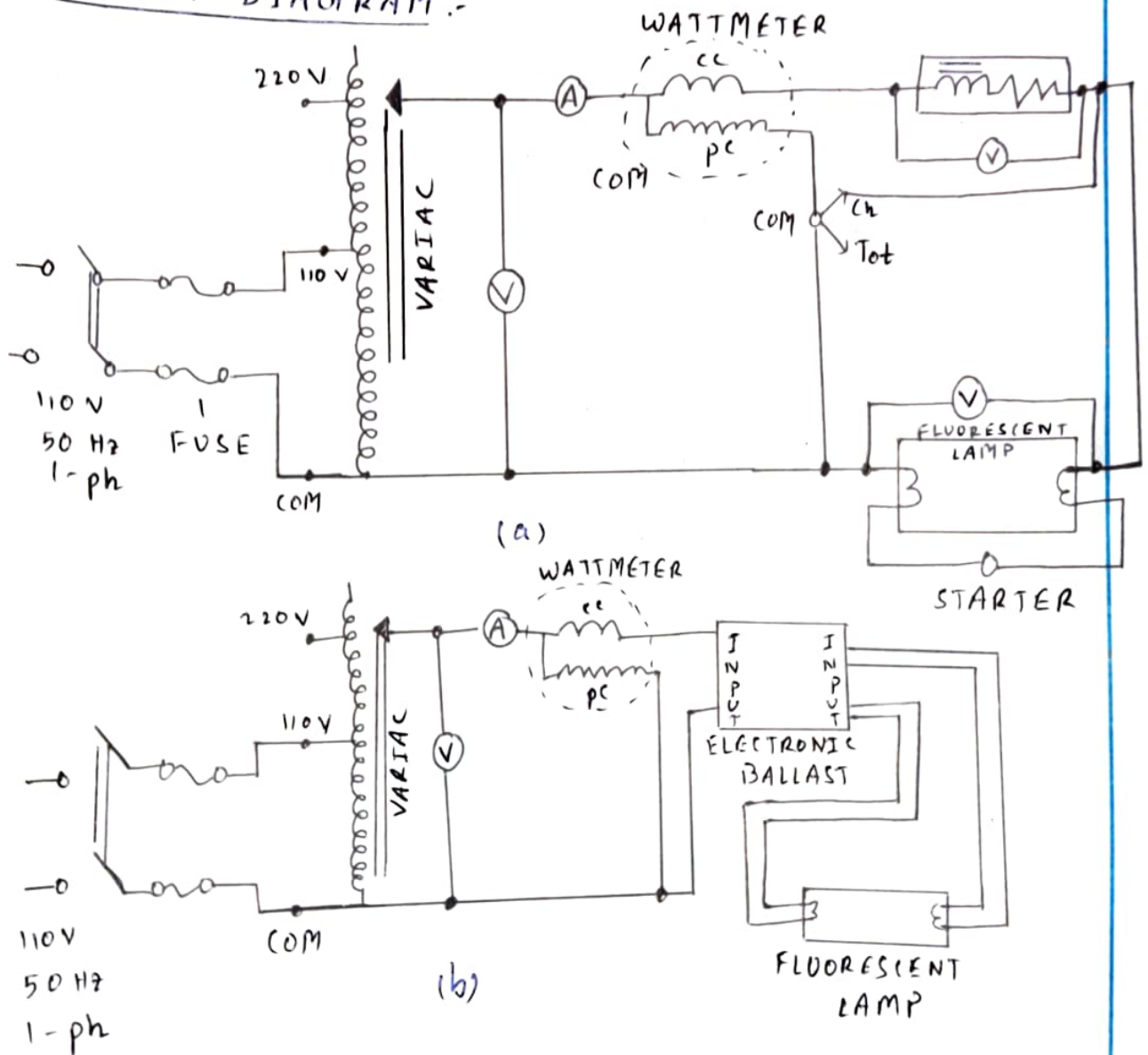

APPARATUS LIST:

Sl. No.	APPARATUS	QTY	RANGE/RATING	MAKER'S NAME	MAKER'S NO.
1.	AC Voltmeter	3	1) 0-150, 0-300, 0-600 V 2) 0-150, 0-300, 0-600 V 3) 0-150, 0-300, 0-600 V	1) MECO-V 2) Automatic E.L. 3) Automatic E.L.	1) 8554 2) 2/76/7855/2 3) MHCEB305
2.	Ammeter	1	0-1 0-2	Automatic Electric Ltd.	10/41/15247/46
3.	Wattmeter	1	0-150	MECO-V	3534/2/23
4.	Fluorescent bulb	1	40W, 56 Hz, 220 V	Philips	-
5.	choke				
	(i) Inductive Ballast	1	TLP 36/1 x TL 40W	Philips	-
	(ii) Electronic Ballast	1	TLD 18/2 x TL 20W	Philips	-
6.	STARTER	1	20-65 W	Philips	-
7.	VARIAC	1	0-270 W	Automatic Electric Limited	1210/052339/47

OBSERVATIONS AND CALCULATIONS:RUN - I

Striking voltage = 200 V

Supply voltage V_s (V)	Line current I_L (A)	Voltage across F.L. V_{FL} (V)	Voltage across choke V_{Ch} (V)	Power consumed by Ballast P_{Ch} (W)	Total power consumed P_T (W)	Power consumed by F.L. (W) $(P_{FL} = P_T - P_{Ch})$	Total power factor $(= \frac{P_T}{V_s I_L})$	Power factor of choke $(= \frac{P_{Ch}}{V_{Ch} I_L})$	Power factor of F.L. $(= \frac{P_{FL}}{V_{FL} I_L})$
200	0.21	122	128	8	26	18	0.619	0.298	0.702
206	0.24	121	136	8	36	28	0.722	0.245	0.964
210	0.25	122	142	10	35	25	0.666	0.282	0.820
215	0.27	120	150	10	38	28	0.655	0.247	0.864
220	0.28	120	156	12	40	28	0.644	0.275	0.833
225	0.29	119	164	12	41	29	0.628	0.252	0.840
230	0.30	119	170	14	42	28	0.609	0.274	0.784

Extinguish Voltage = 150 V

RUN-2

Striking voltage = 48 V

Supply voltage (V_i) (in V)	Line current (I_L) (in A)	Wattmeter (P_T) (in W)	Power factor $= \frac{P_T}{V_i \cdot I_L}$
230	0.17	38	0.972

Extinguish Voltage = 20 V

Comparison at 230 V (V_i)

Supply Voltage (V_i) (V)	Input current (I_L) (A)	Total power consumed (P_T) (W)	Power factor $= \frac{P_T}{V_i \cdot I_L}$
Run 1 230	0.3	42	0.609
Run 2 230	0.17	38	0.972

Reasons:-

The electronic ballast circuit has power factor approximately 1. On the other hand, inductive ballast circuit has power factor very less than 1. Thus, electronic ballast circuit is more efficient, utilizing power more efficiently than inductive ballast circuit.


Scale:-

Along x-axis,

1 S.D. = 0.1 V

Along y-axis,

1 S.D. = 0.02 A

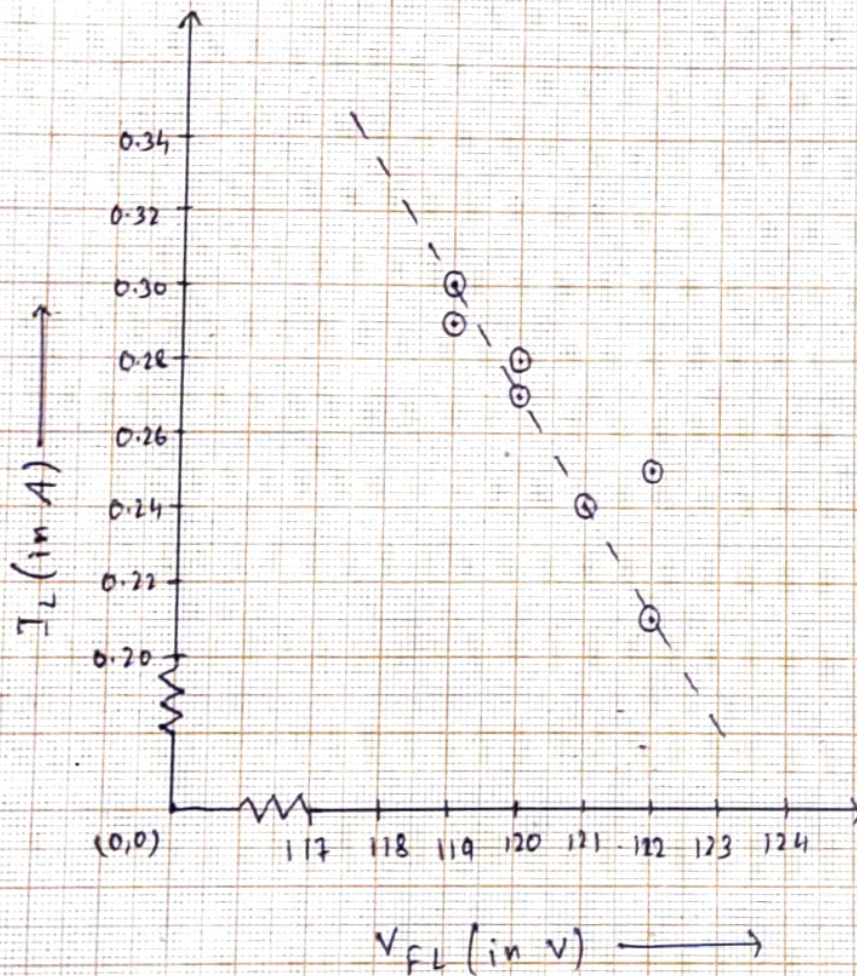


I_L vs. V_{FL} curve for fluorescent lamp


Scale:-

Along x-axis,
10 S.D. = 10 V

Along y-axis,
10 S.D. = 0.02 A

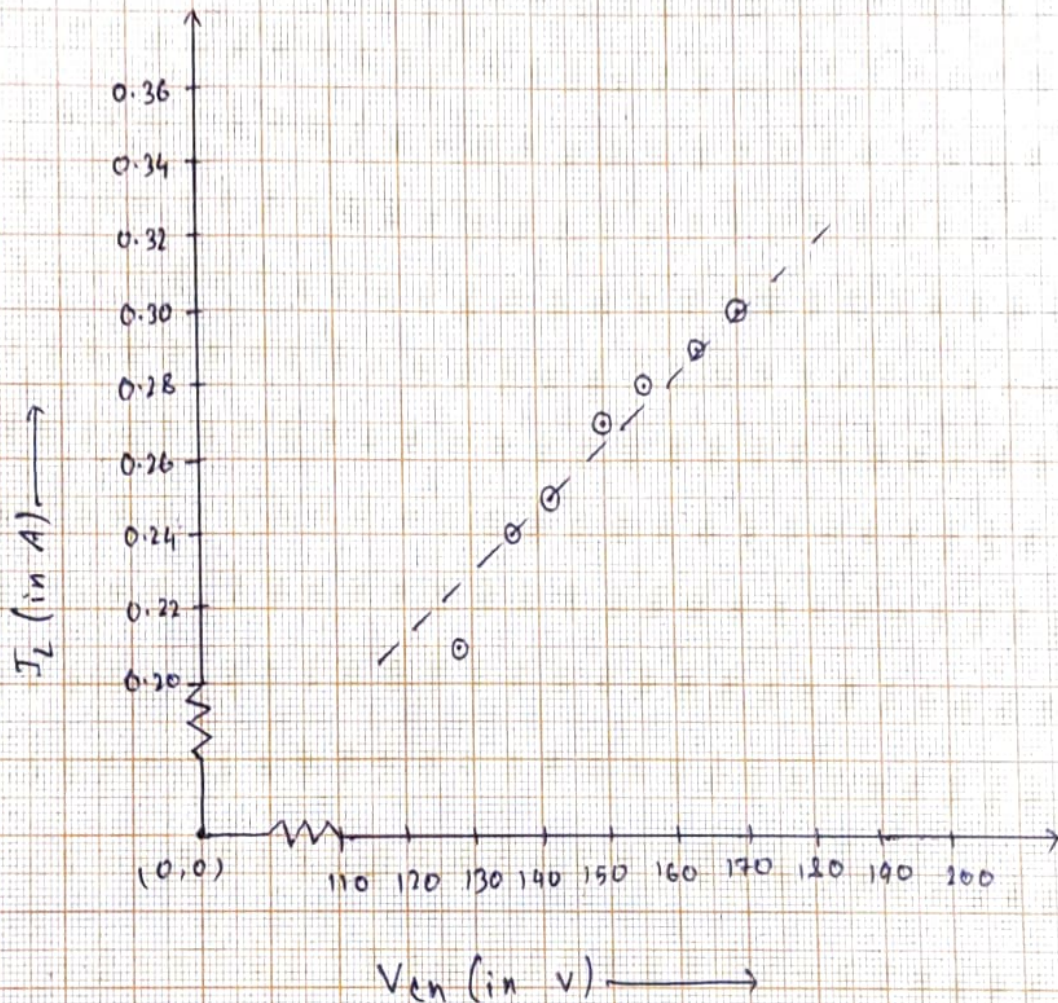

I_L vs. V_L curve for choke coil

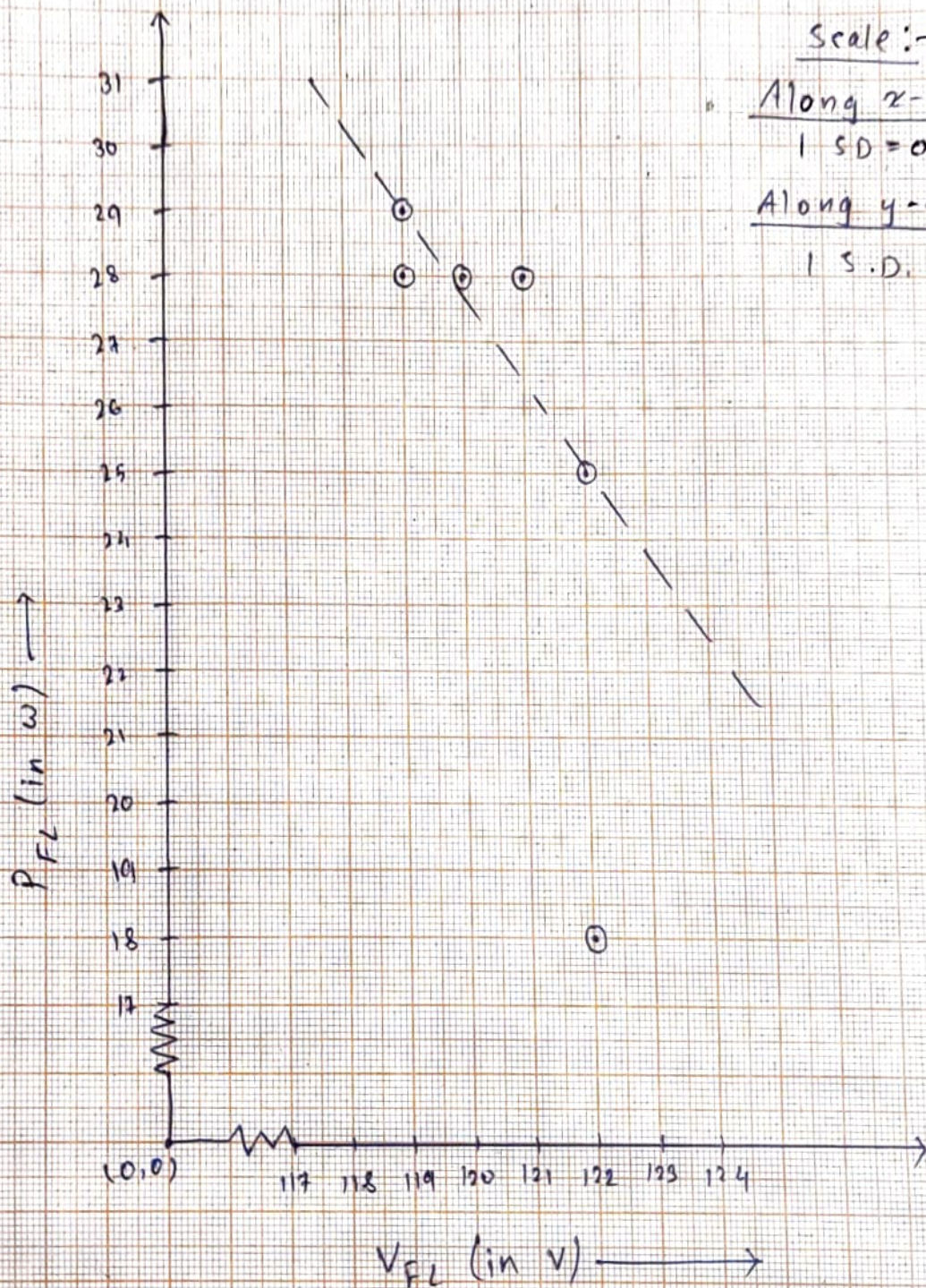

P_{FL} vs V_{FL} curve for fluorescent Lamp


Scale:-

Along x-axis,

1 S.D. = 1 V

Along y-axis,

1 S.D. = 0.1 W

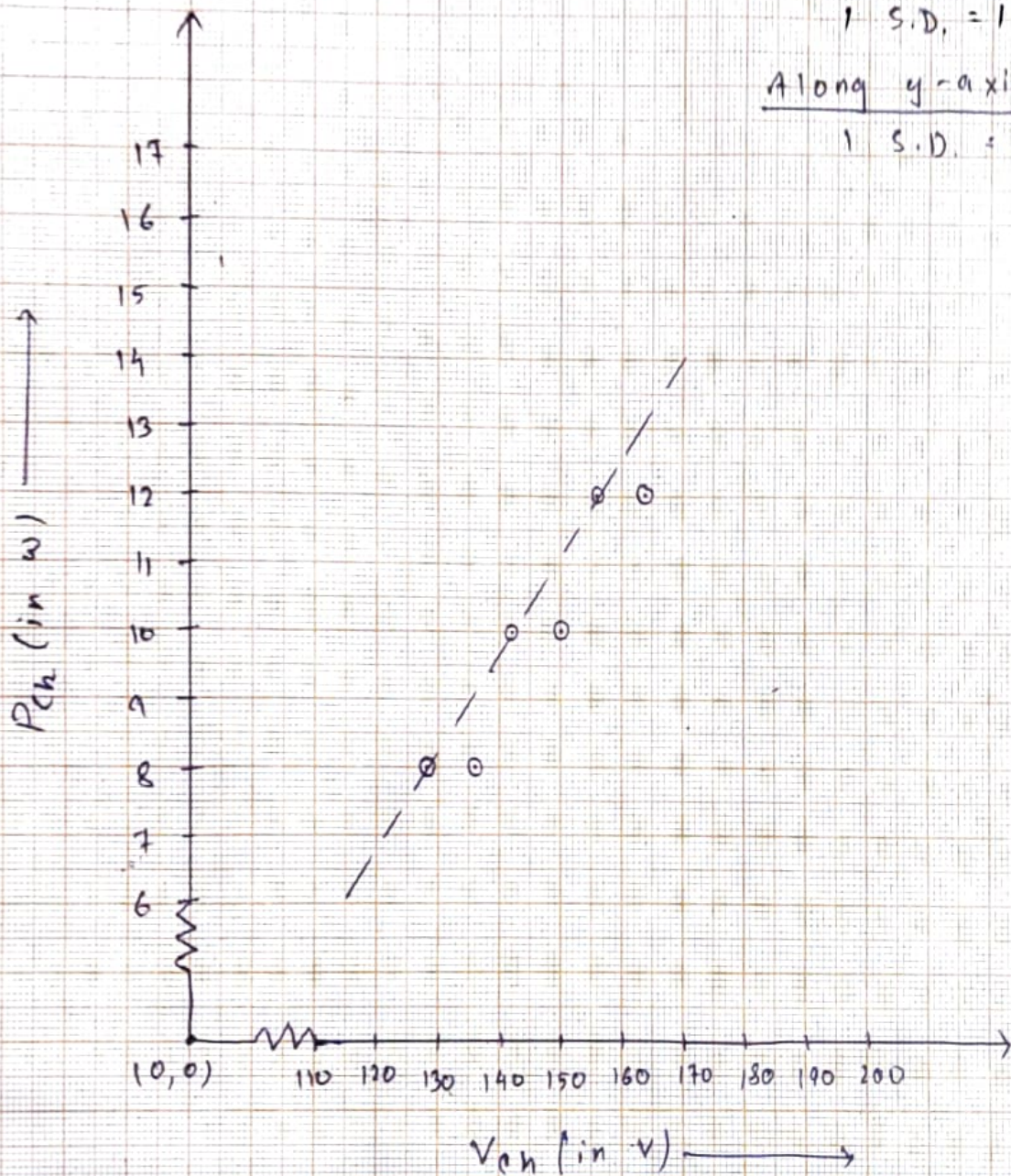

P_{ch} vs V_{ch} curve for choke coil