

JADAVPUR UNIVERSITY

Faculty of Engineering & Technology

.....Electronics..... Engg. Laboratory

Name TATHAGATA SUR

Class CSE-VG1 Sec. A1 Roll No. 009210301030

Date of Experiment...22/01/24..... Date of Submission...29/01/24.....

Marks Obtained..... Signature of Examiner.....

NAME _____

CO-WORKER

ROLL

Shyam Sundar Karmakar 002310501025

Samim Sekh 002310501026

Pratyay Kar 002310501027

Jayosmit Pal 002310501028

Abir Chakraborty 002310501629

Anirudh Modi 002310501031

Experiment No. 04-A

Commence at.....11:00 AM.....

Completed at.....2:00 PM

Name of Teacher concerned

TITLE: Truth table of basic logic gates and
NAND gate as a Universal Logic gate

OBJECT: To study T-Tb of basic gates and NAND gate as Universal gate

Apparatus used:-

- (i) IC - 7400 (ii) Regulated DC power supply
 (iii) Bread board (iv) LED (v) Resistor



IC - 7400:

The series of transistor logic IC are now very power and are quickly replacing diode transistor logic. It has 14 pins and 4 inbuilt NAND gates.


Input pairs:- 1 & 2, 4 & 5, 9 & 10, 12 & 13

Output pairs:- 3, 6, 8, 11

Pin 7 is earthed and 14 is connected to voltage Source.

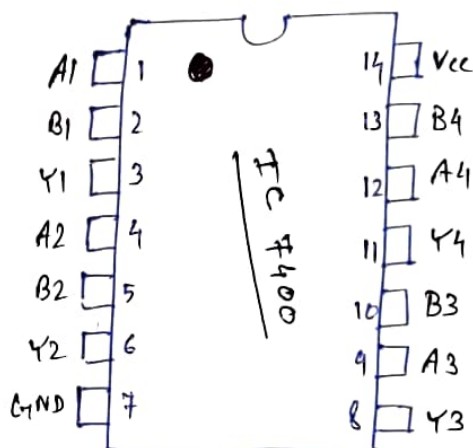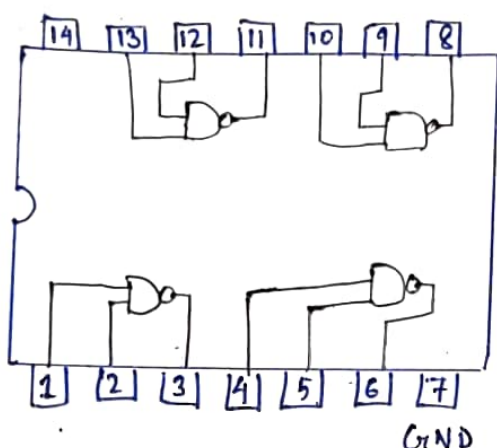Universal gate:-

NAND and NOR gates are called universal gates as they can be used to construct any Boolean function without using any other gate. They are economical to fabricate into circuits.

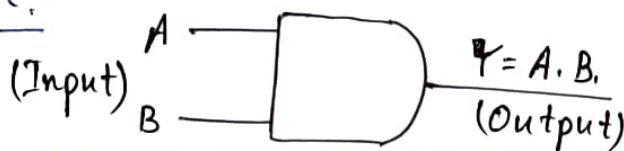
AND gate:-

Truth Table:-

SL No.	A	B	$Y = A \cdot B$
1>	0	0	0
2>	0	1	0
3>	1	0	0
4>	1	1	1


Using NAND gate:-

SL.No.	A	B	$\overline{A \cdot B}$	$\overline{\overline{A \cdot B}} = A \cdot B$
1>	0	0	1	0
2>	0	1	1	0
3>	1	0	1	0
4>	1	1	0	1

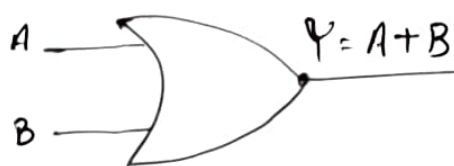OR gate:-Truth Table:-


SL.No.	A	B	$Y = A + B$
1>	0	0	0
2>	0	1	1
3>	1	0	1
4>	1	1	1

Using NAND gate:-

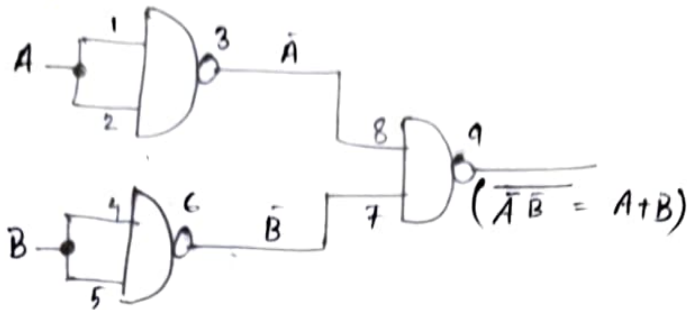

Sl.No.	A	B	\bar{A}	\bar{B}	$\bar{A} \cdot \bar{B} = A+B$
1)	0	0	1	1	0
2)	0	1	1	0	1
3)	1	0	0	1	1
4)	1	1	0	0	1


NOT gate:-

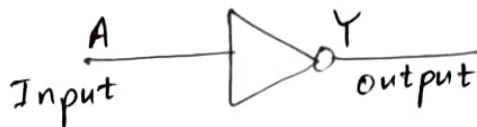

Truth Table:-

Sl.No.	A	$Y = \bar{A}$
1)	0	1
2)	1	0

Using NAND gate:-

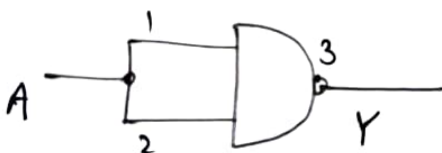

Observations:

- 1) For 1, we take inputs in pin (1,2), (4,5), (9,10), (12,13) and outputs from 3, 6, 8, 11 respectively. The LED bulb glows for all order of high and low inputs except when both inputs are of high voltage.
- 2) For 2, we take (1,2) as input and 3 as output. We then connect output to (4,5) input pins and take output γ from 6. We see that the bulb glows only when both inputs are high pass, thus it is equivalent to AND gate.
- 3) For 3, we take (1,2) and (4,5) as input pins, and 3, 7 as their respective outputs are used as inputs for (9,10), giving resultant output γ through 8. It is observed that LED stops glowing only for both low inputs, hence equivalent to OR gate.
- 4) For 4, we take either a high pass or a low pass input for this case, and observe that we get the opposite pass of the input; hence equivalent to NOT gate.

Precautions:-

- (i) All pins must be correctly identified from I.C.
- (ii) All connections on bread board must be properly made
- (iii) The V_{cc} of 5V should not cross limit
- (iv) All wires must be properly insulated.