

JADAVPUR UNIVERSITY

Faculty of Engineering & Technology

...Electronics... Engg. Laboratory

Name TATHAGATA SUR

Class CSE-VG1 Sec. A1 Roll No. 002310501030

Date of Experiment 08/01/2024 Date of Submission 15/01/2024

Marks Obtained Signature of Examiner

NAME

CO-WORKER

ROLL

Shyam Sunder Karmakar

002310501025

Samim Sekh

002310501026

Pratyay Kar

002310501027

Joyosmit Pal

002310501028

Abin Chakraborty

002310501029

Ankit Shaw

~~002310501030~~

Anirudh Modi

002310501031

Experiment No. 02-B

Commence at 11:00 AM

Completed at 2:00 PM

Name of Teacher concerned

TITLE: I-V characteristics of Zener-diode under reverse biased condition.


OBJECT: To study the current-voltage characteristics of a reverse biased Zener diode by plotting I-V graph and to become familiar with its breakdown char. and measure the Zener breakdown voltage.

Theory:-

A Zener diode is constructed for operation in the reverse breakdown region. It is used as a voltage regulator. The relation between $I-V$ is almost linear in this case.

After reaching a certain voltage, called the 'Breakdown Voltage', the current increases widely even for a small change in the voltage. This happens due to "Avalanche Breakdown" and the "Zener-effect" of the Zener Diode. However, there is no appreciable change in voltage. After the Zener potential (V_Z), current increases exponentially.

Circuit Diagram:-

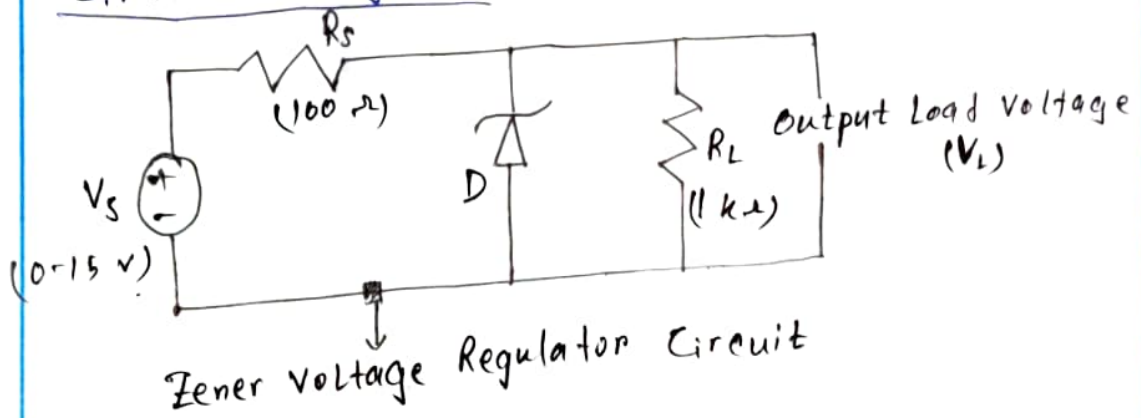

Apparatus Used:-

- 1) DC power supply
- 2) Ammeter
- 3) Bread Board
- 4) Zener-Diode
- 5) Voltmeter
- 6) Connection Wires

Observation Table:-Zener Diode

No. of obs.	Reverse Voltage (V_R) in V	Reverse Current (I_R) in μA
1)	2.7	0.1
2)	3	0.2
3)	4.2	0.3
4)	5.4	0.5
5)	6	160
6)	6.3	180

Conclusion:-

The Reverse Breakdown Voltage for Zener diode = 5.2 V

(It depends on several factors like semiconductor material, doping level, etc.)

Zener Diode


Scale:-

Along X-axis,

1 ssd = 0.1 V

Along Y-axis,

1 ssd = 2 μ A

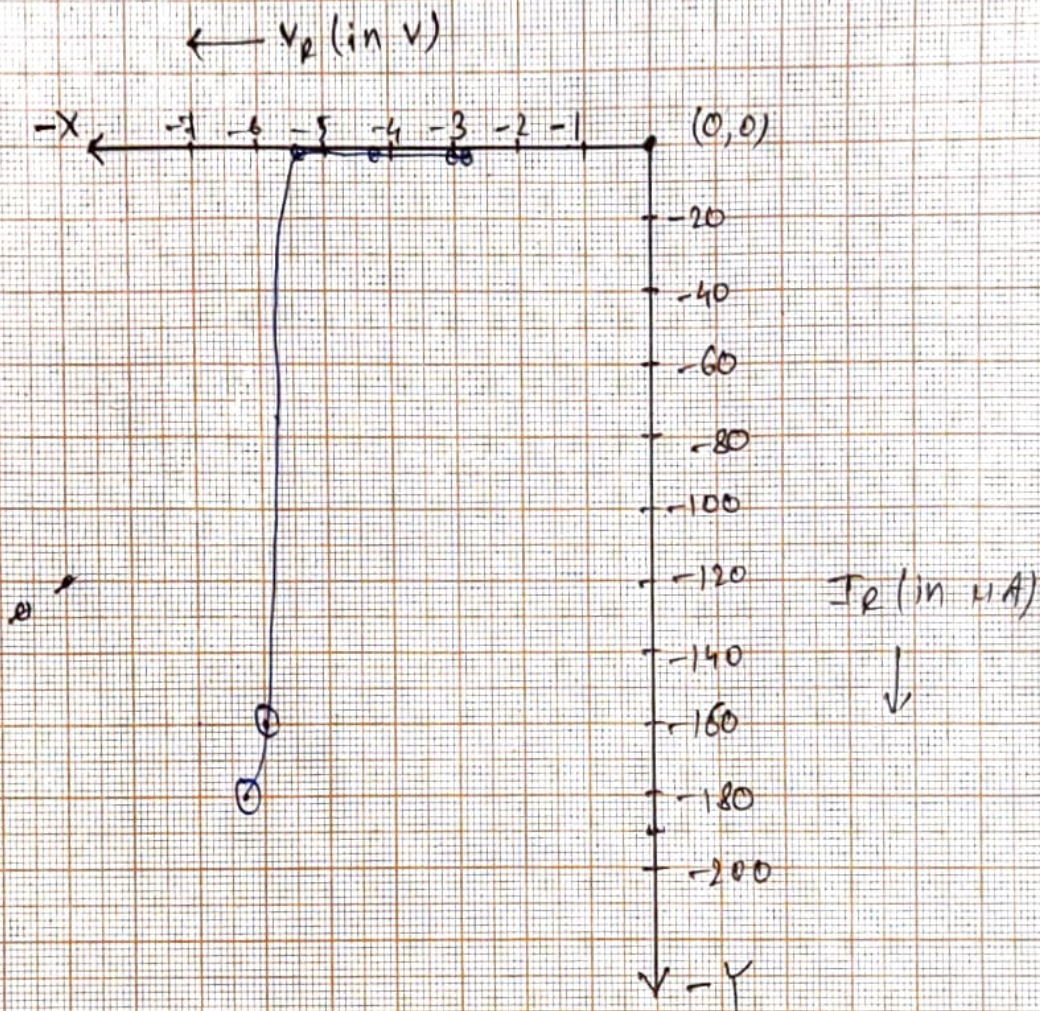

I-V graph of Zener Diode in R.B.